

139/2208/2013 SPH 336 REPORT

INTRODUCTION

In this semester we learned system-level modeling using systemc. Systemc is a set of c++ classes and macros which provide simulation interface.

LANGUAGE FEATURES

systemc comprises of the following features:

Modules

Modules are the basic building blocks of a systemc design hierarchy. A systemc model usually consists of several modules which communicate via ports.

Ports

Ports allow communication from inside a module to the outside(usually to other modules) via channels.

Exports

Exports incorporate channels and allow communication from inside a module to the outside(usually to other modules).

Processes

Processes are the main computation elements. They are concurrent

Channels

Channels are the communication elements. They can be either simple wires or complex communication mechanisms like FIFOs or bus channels.

The channels are:

- signal
- buffer
- FIFO
- mutex
- semaphore

Interfaces

Ports use interfaces to communicate with channels

Events

Events allow synchronization between processes and must be defined during initialization

139/2208/2013 SPH 336 REPORT

SYSTEMC PROJECT 1

in this project I was supposed to modify the design of the 1 by 2 decoder to 2 by 4 decoder.

TRUTH TABLES

1 by 2 decoder


A	D ₁	D ₀
0	0	1
1	1	0

2 by 4 decoder

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

MODULES

The module diagram is as shown below:

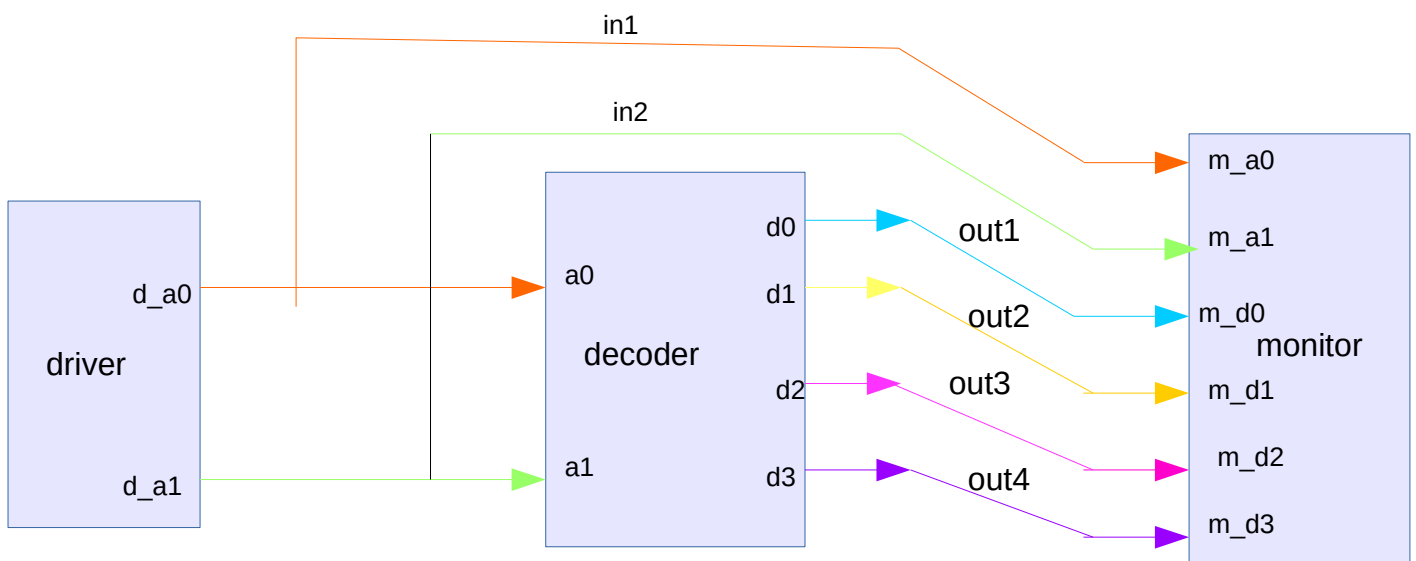

- driver: this module produced the input signals for the decoder.
- Decoder: implemented the working of the decoder

139/2208/2013 SPH 336 REPORT

- monitor: displayed the variation of signals in the program.

FILES DESCRIPTION

driver2.h

This file defined the driver module

I declared two output ports of type bool named `d_a0` and `d_a1`.

The function `drive` was to run in a while loop sending a combination of `1s` and `0s` to the `decoder` module.

decoder2.h

This file defined the decoder module

I declared two input ports of type bool as `a0` and `a1` and four output ports as `d0,d1,d2,d3`.

The implementation of the decode function is as follows:

- if input `a0` was 0 and input `a1` 0, output `d1,d2`, and `d3` were to be 0 and `d0` to be 1.
- if input `a0` was 1 and input `a1` 0, output `d0,d2` and `d3` were to be 0 and `d1` to be 1.
- if input `a0` was 0 and input `a1` 1, output `d0,d1` and `d3` were to be 0 and `d2` to be 1.
- if input `a0` was 1 and input `a1` 1, output `d0,d1` and `d2` were to be 0 and `d3` to be 1.

monitor2.h

This file defined the monitor module

I declared six input ports of type bool as `m_a0,m_a1,m_d0,m_d1,m_d2` and `m_d3`

the function `monita` was to output the values read from the ports.

decoder2.cc

this file implemented the connection between the three modules.

I defined six signals of type bool as `in1,in2, out1, out2,out3` and `out4`.

I connected the corresponding ports as shown in the diagram above using the signals.

I also declared a trace file `ft` and a timing diagram file called `timing_diagram` to be used in the simulation.


makefile

This file automated the process of compiling the different files and linking their object files into an executable called decoder.

139/2208/2013 SPH 336 REPORT

SIMULATION

 For the simulation I used [gtkwave](#) and the output is as shown below.



RESULTS FROM THE SIMULATION

The results from the simulation are as shown below:

```
decoder : bash - Konsole
File Edit View Bookmarks Settings Help
root@berniegach: ~/karibe/cplusplus_examples/Benard/decoder# ./decoder
SystemC 2.3.1-Accellera --- Oct 26 2015 14:39:22
Copyright (c) 1996-2014 by all Contributors.
ALL RIGHTS RESERVED

Info: (1703) tracing timescale unit set: 1 ns (timing_diagram.vcd)
at 0 s inputs are: 0 and 0 outputs are: 1 and 0 and 0 and 0
at 10 ns inputs are: 0 and 1 outputs are: 0 and 0 and 1 and 0
at 15 ns inputs are: 1 and 1 outputs are: 0 and 0 and 0 and 1
at 20 ns inputs are: 1 and 0 outputs are: 0 and 1 and 0 and 0
root@berniegach: ~/karibe/cplusplus_examples/Benard/decoder#
```


139/2208/2013 SPH 336 REPORT

SYSTEMC PROJECT 2

In this project, I was supposed to design a sequential circuit of my choice using systemc and simulate it. I chose an S-R flip-flop as my circuit.

SEQUENTIAL CIRCUIT DIAGRAM

 
The circuit diagram for the sequential circuit is shown below:



MODULES

The module diagram is as shown below:

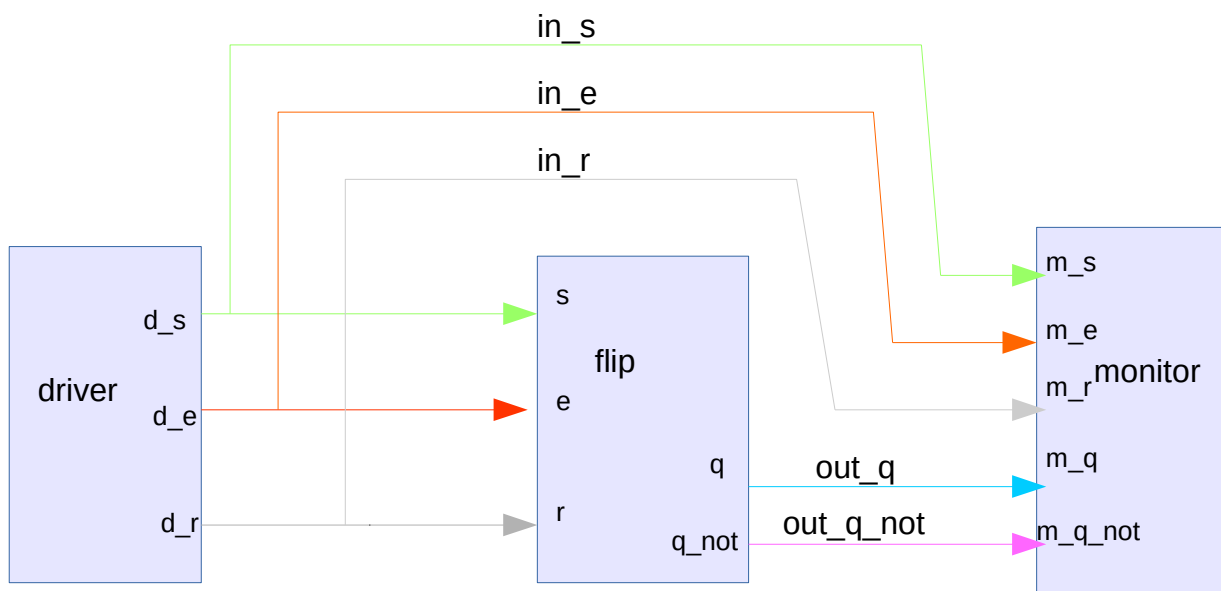I used vi as my c++ editor and g++ as the compiler.
The module diagram is as shown below:



- driver: this modules produced the input signals for the flip flop
- flip: this module implemented the working of the flip flop
- monitor: this module displayed the variation of signals present in the program

FILES DECRPTION

139/2208/2013 SPH 336 REPORT

For this project, I used five different files to make the sequential circuit. These are

driver_seq.h

This file defined the driver module

I declared three output ports of type bool as `d_s`, `d_r` and `d_e`.

I named the only function as `drive` and it was supposed to run in a while loop sending a combination of 1 and 0 to the flip module with a wait of 5ns.

seque.h

This file defined the flip module.

I declared three output ports of type bool as `s`, `e` and `r` and two output ports of of type bool as `q` and `q_not`.

I declared the function as `flip_do` and its operation is as follows:

1. read the signals from `s` and `e`, carry out the boolean `and` on them, do the boolean `not` on the result and store in a temporary variable `temp1`.
2. read the signals from `e` and `r`, carry out the boolean `and` on them, do the boolean `not` on the result and store the result in a temporary variable `temp2`.
3. read the signal from `q_not`, do the boolean `and` with variable `temp1`, do the boolean `not` on the result and store the result in variable `q`.
4. read the signal from `q`, do the boolean `and` with variable `temp2`, do the boolean `not` on the result and store the result in variable `q_not`.

monitor_seq.h

This file defined the monitor module

I declared five input ports of type bool as `m_e`, `m_s`, `m_r`, `m_q` and `m_q_not`.

The function `monita` was to output the values read from this ports

seque.cc

This file implemented the connection between the three modules.

I declared five signals of type bool as `in_s`, `in_e`, `in_r`, `out_q` and `out_q_not`.

I connected the corresponding ports as shown in the diagrams using the signals.

I also declared a trace file `ft` and a timing diagram file called `timing_diagram` to be used in the simulation.


makefile

This file automated the process of compiling the different files and linking their object files into an executable called `seque`.

139/2208/2013 SPH 336 REPORT

SIMULATION

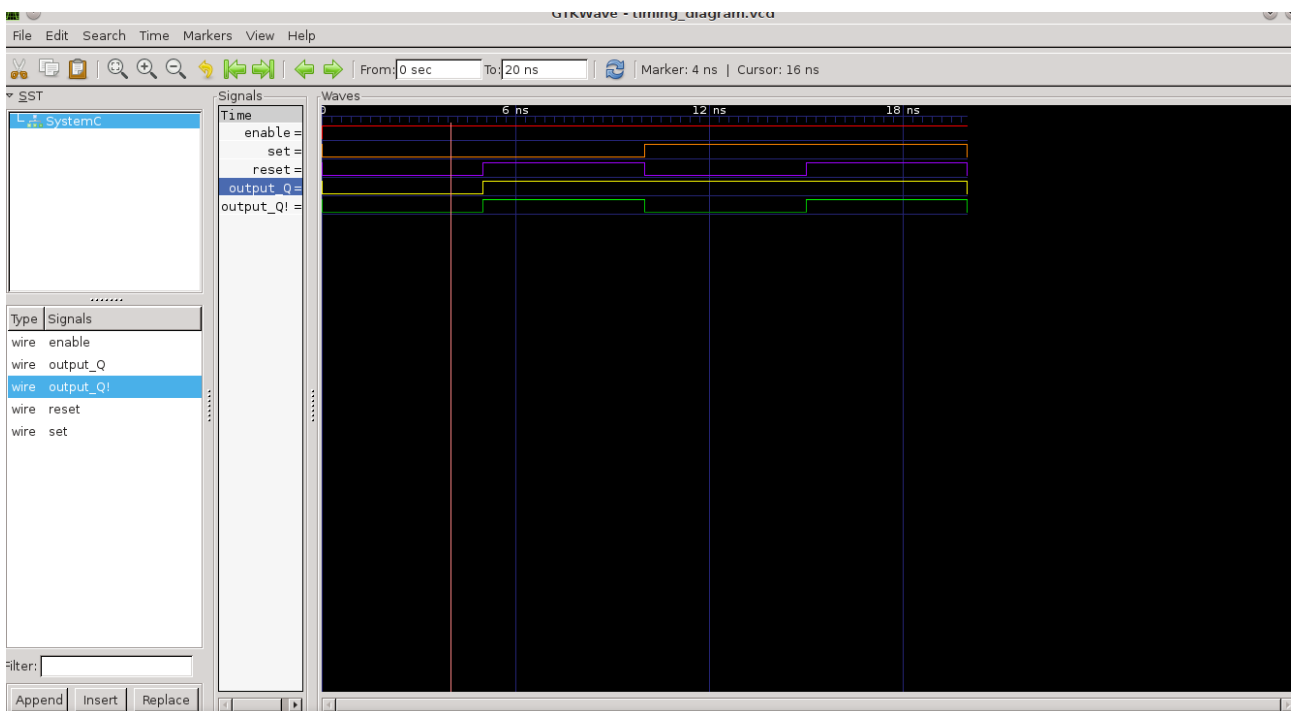For the simulation I used [gtkwave](#) and the output is as shown below.



EXPECTED RESULTS


The theoretical expected results from the simulation is as shown in the table below.

Inputs			Outputs		Comments
E	S	R	Q_{n+1}	$\overline{Q_{n+1}}$	
1	0	0	Q_n	$\overline{Q_n}$	No change
1	0	1	0	1	Rset
1	1	0	1	0	Set
1	1	1	x	x	Indeterminate

139/2208/2013 SPH 336 REPORT

RESULTS FROM THE SIMULATION

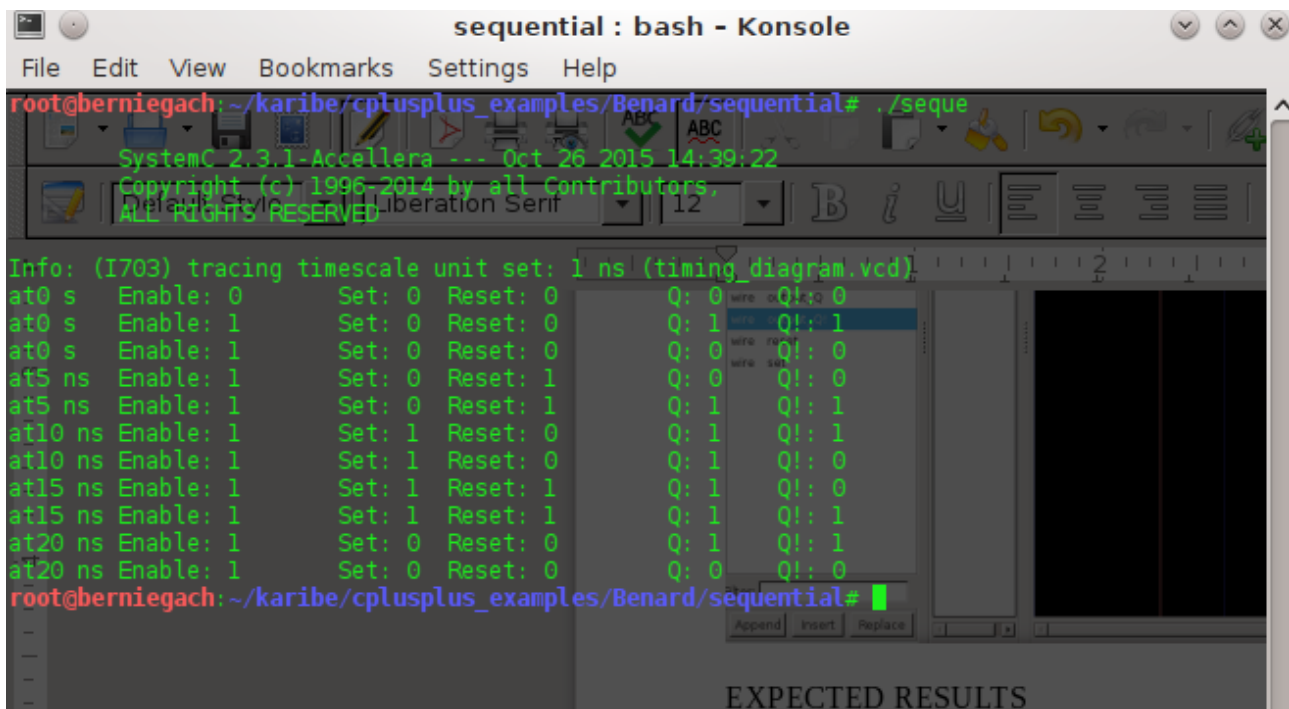The results from the simulation are as shown below



```
sequential : bash - Konsole
File Edit View Bookmarks Settings Help
root@berniegach: ~/karibe/cplusplus_examples/Benard/sequential# ./seque
SystemC 2.3.1-Accellera --- Oct 26 2015 14:39:22
Copyright (c) 1996-2014 by all Contributors.
ALL RIGHTS RESERVED

Info: (I703) tracing timescale unit set: 1 ns (timing_diagram.vcd)
at0 s Enable: 0 Set: 0 Reset: 0 Q: 0 Q!: 0
at0 s Enable: 1 Set: 0 Reset: 0 Q: 1 Q!: 1
at0 s Enable: 1 Set: 0 Reset: 0 Q: 0 Q!: 0
at5 ns Enable: 1 Set: 0 Reset: 1 Q: 0 Q!: 0
at5 ns Enable: 1 Set: 0 Reset: 1 Q: 1 Q!: 1
at10 ns Enable: 1 Set: 1 Reset: 0 Q: 1 Q!: 1
at10 ns Enable: 1 Set: 1 Reset: 0 Q: 1 Q!: 0
at15 ns Enable: 1 Set: 1 Reset: 1 Q: 1 Q!: 0
at15 ns Enable: 1 Set: 1 Reset: 1 Q: 1 Q!: 1
at20 ns Enable: 1 Set: 0 Reset: 0 Q: 1 Q!: 1
at20 ns Enable: 1 Set: 0 Reset: 0 Q: 0 Q!: 0
root@berniegach: ~/karibe/cplusplus_examples/Benard/sequential#
```

EXPECTED RESULTS

OBSERVATION

In the first project, the results from the simulation were the same as those in the truth table.

The project was successfully done.

The results from the simulation in project 2 were not fully the same as the expected results. There was some variation. This source of this error is the implementation of the flip_do method in [seque.h](#) file.

CONCLUSION

The objective of the unit was to teach me the skills of system modeling using [systemc](#). Although in the last project the obtained results varied from the expected results I was still successful in learning how to use the systemc libraries to model various systems and do interpretation from the results obtained after simulation with [gtkwave](#) accordingly.